

Міністерство освіти і науки України  
Національний університет „Львівська політехніка”

Кафедра ЕОМ



## Звіт

з лабораторної роботи №3

з дисципліни: “Моделювання комп’ютерних систем”

на тему: “Поведінковий опис цифрового автомата. Перевірка роботи автомата  
за допомогою стенда Elbert V2 - Spartan 3A FPGA.”

Варіант №9

Виконав:  
ст. гр. КІ-201  
Іванюк О.О.

Прийняв:  
Козак Н.Б.

Львів - 2023

### Мета роботи:

На базі стенда Elbert V2 - Spartan 3A FPGA реалізувати цифровий автомат для обчислення значення виразу дотримуючись наступних вимог:

1. Функціонал пристрою повинен бути реалізований згідно отриманого варіанту завдання. Дивись розділ ЗАВДАННЯ.
2. Пристрій повинен бути ітераційним (АЛП (ALU) повинен виконувати за один такт одну операцію), та реалізованим згідно наступної структурної схеми (Малюнок 1).

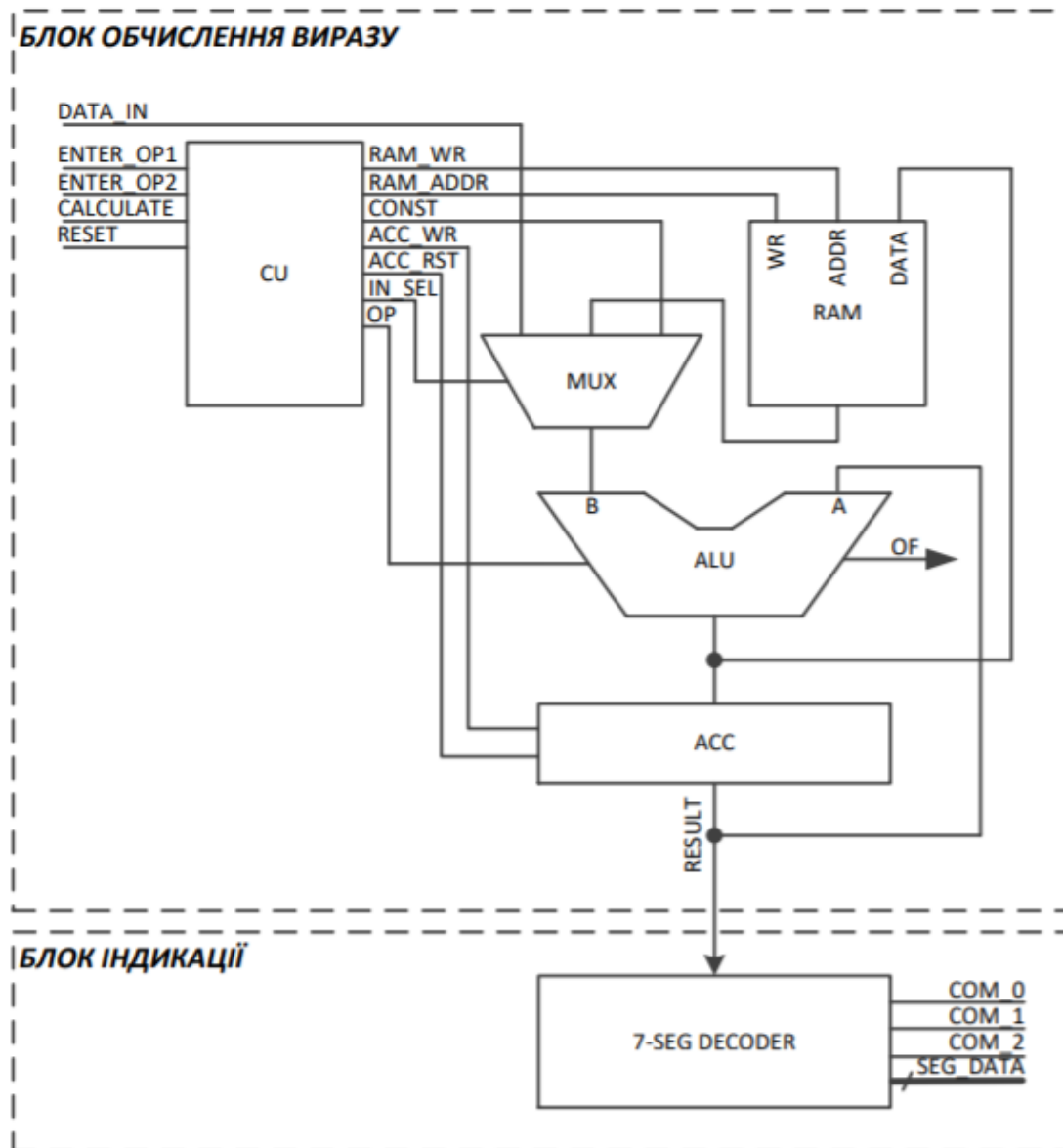


Рис. 1 - Структурна схема автомата.

### Завдання:


ВАРІАНТ	ВИРАЗ
9	$((OP2 - 4) + OP1) \text{ or } 2$

## Виконання:

1) Створив файл MUX.vhd.

```
1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3
4  entity my_MuX_intf is
5  port (
6      DATA_IN          : in std_logic_vector(7 downto 0);
7      IN_SEL             : in std_logic_vector(1 downto 0);
8      CONSTANT_BUS1     : in std_logic_vector(7 downto 0);
9      CONSTANT_BUS2     : in std_logic_vector(7 downto 0);
10     RAM_DATA_OUT_BUS   : in std_logic_vector(7 downto 0);
11     IN_SEL_OUT_BUS     : out std_logic_vector(7 downto 0)
12 );
13 end my_MuX_intf;
14
15 architecture my_MuX_arch of my_MuX_intf is
16 begin
17     INSEL_A_MUX: process(DATA_IN, CONSTANT_BUS1, CONSTANT_BUS2, RAM_DATA_OUT_BUS, IN_SEL)
18     begin
19         if (IN_SEL = "00") then
20             IN_SEL_OUT_BUS <= DATA_IN;
21         elsif (IN_SEL = "01") then
22             IN_SEL_OUT_BUS <= RAM_DATA_OUT_BUS;
23         elsif (IN_SEL = "10") then
24             IN_SEL_OUT_BUS <= CONSTANT_BUS1;
25         else
26             IN_SEL_OUT_BUS <= CONSTANT_BUS2;
27         end if;
28     end process INSEL_A_MUX;
29 end my_MuX_arch;
```

Рис.1. Реалізація мультиплексора у файлі MUX.vhd

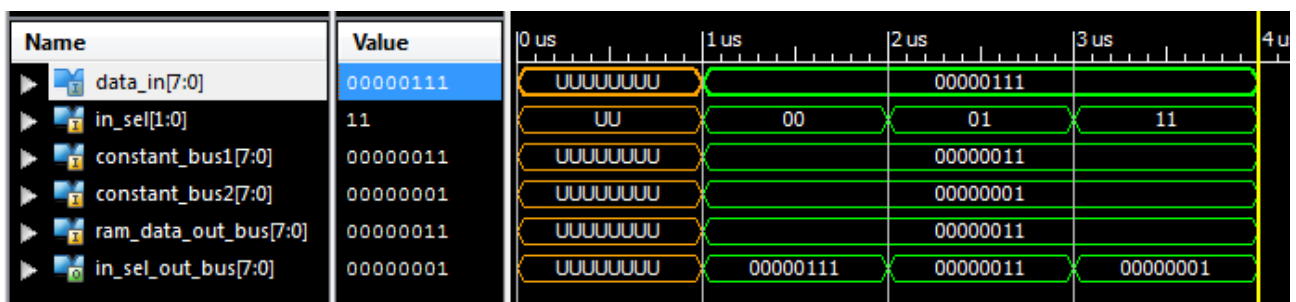

Симуляція роботи мультиплексора


2) Створив файл ACC.vhd.

```

1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3
4
5  entity my_ACC_intf is
6  port (
7      CLOCK          : in std_logic;
8      ACC_WR          : in std_logic;
9      ACC_RST         : in std_logic;
10     ACC_DATA_IN_BUS  : in std_logic_vector (7 downto 0);
11     ACC_DATA_OUT_BUS : out std_logic_vector (7 downto 0)
12 );
13 end my_ACC_intf;
14
15 architecture my_ACC_arch of my_ACC_intf is
16
17     signal ACC_DATA: std_logic_vector (7 downto 0);
18
19     begin
20
21     ACC : process (CLOCK, ACC_DATA)
22     begin
23         if (rising_edge(CLOCK)) then
24             if (ACC_RST = '1') then
25                 ACC_DATA <= "00000000";
26             elsif (ACC_WR = '1') then
27                 ACC_DATA <= ACC_DATA_IN_BUS;
28             end if;
29         end if;
30         ACC_DATA_OUT_BUS <= ACC_DATA;
31     end process ACC;
32
33 end my_ACC_arch;

```

Рис.2. Реалізація регістра АСС у файлі ACC.vhd

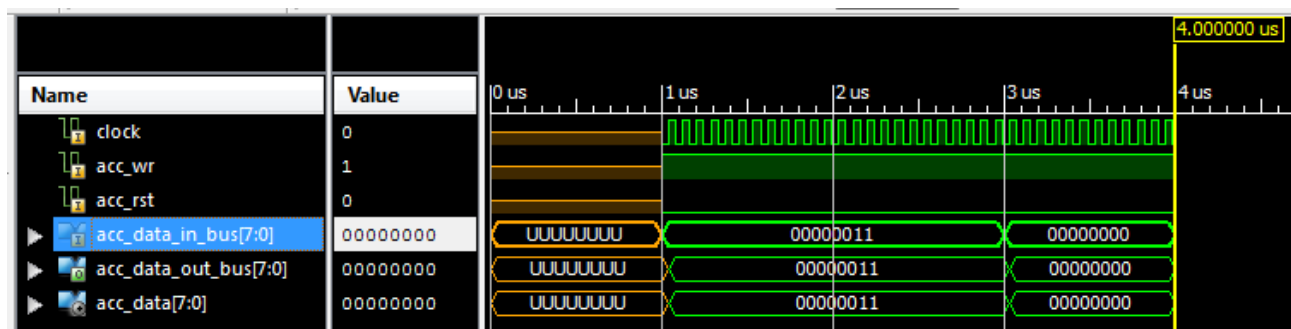

Симуляція роботи регістра


- 3) Визначив набір необхідних операцій для виконання виразу згідно свого варіанту і реалізував АЛП(ALU) у файлі ALU.vhd з підтримкою визначеного набору операцій (рис.3).

```

1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3  use IEEE.NUMERIC_STD.ALL;
4  use IEEE.STD_LOGIC_UNSIGNED.ALL;
5
6  entity my_ALU_intf is
7  port (
8      OP_CODE_BUS      : in std_logic_vector (1 downto 0);
9      IN_SEL_OUT_BUS   : in std_logic_vector (7 downto 0);
10     ACC_DATA_OUT_BUS  : in std_logic_vector (7 downto 0);
11     ACC_DATA_IN_BUS   : out std_logic_vector (7 downto 0)
12 );
13 end my_ALU_intf;
14
15 architecture my_ALU_arch of my_ALU_intf is
16 begin
17
18     ALU : process (OP_CODE_BUS, IN_SEL_OUT_BUS, ACC_DATA_OUT_BUS)
19         variable A: unsigned (7 downto 0);
20         variable B: unsigned (7 downto 0);
21     begin
22         A := unsigned (ACC_DATA_OUT_BUS);
23         B := unsigned (IN_SEL_OUT_BUS);
24
25         case (OP_CODE_BUS) is
26             when "00" => ACC_DATA_IN_BUS <= STD_LOGIC_VECTOR (B);
27             when "01" => ACC_DATA_IN_BUS <= STD_LOGIC_VECTOR (A + B);
28             when "10" => ACC_DATA_IN_BUS <= STD_LOGIC_VECTOR (A - B);
29             when "11" => ACC_DATA_IN_BUS <= STD_LOGIC_VECTOR (A or B);
30             when others => ACC_DATA_IN_BUS <= "00000000";
31         end case;
32     end process ALU;
33
34 end process ALU;
35
36 end my_ALU_arch;

```

Рис.3. Реалізація АЛП(ALU) у файлі ALU.vhd з підтримкою визначеного набору операцій.

 

Симуляція роботи АЛП

4) Визначив множину станів і реалізував пристрій керування (CU) у файлі CU.vhd.

```
1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3
4  entity my_CU_intf is
5  port(
6  CLOCK      : in std_logic;
7  ENTER_OP1  : in std_logic;
8  ENTER_OP2  : in std_logic;
9  CALCULATE  : in std_logic;
10 RESET      : in std_logic;
11
12 RAM_WR      : out std_logic;
13 RAM_ADDR_BUS : out std_logic_vector(1 downto 0);
14 CONSTANT_BUS1 : out std_logic_vector(7 downto 0);
15 CONSTANT_BUS2 : out std_logic_vector(7 downto 0);
16 ACC_WR      : out std_logic;
17 ACC_RST     : out std_logic;
18 IN_SEL      : out std_logic_vector(1 downto 0);
19 OP_CODE_BUS  : out std_logic_vector(1 downto 0)
20 );
21 end my_CU_intf;
22
23 architecture my_CU_arch of my_CU_intf is
24
25 type cu_state_type is (cu_rst, cu_idle, cu_load_op1, cu_load_op2, cu_run_calc0, cu_run_calc1, cu_run_calc2, cu_run_calc3, cu_finish);
26 signal cu_cur_state : cu_state_type;
27 signal cu_next_state : cu_state_type;
28
29 begin
30
31 CONSTANT_BUS1 <= "00000100";
32 CONSTANT_BUS2 <= "00000010";
33
34 CU_SYNC_PROC: process (CLOCK)
35 begin
36     if (rising_edge(CLOCK)) then
37         if (RESET = '1') then
38             cu_cur_state <= cu_rst;
39         else
40             cu_cur_state <= cu_next_state;
41         end if;
42     end if;
43 end process;
44
45 CUNEXT_STATE_DECODE: process (cu_cur_state, ENTER_OP1, ENTER_OP2, CALCULATE)
46 begin
47     --declare default state for next_state to avoid latches
48     cu_next_state <= cu_cur_state; --default is to stay in current state
49     --insert statements to decode next_state
50     --below is a simple example
51     case(cu_cur_state) is
52         when cu_rst =>
53             cu_next_state <= cu_idle;
54         when cu_idle =>
55             if (ENTER_OP1 = '1') then
56                 cu_next_state <= cu_load_op1;
57             elsif (ENTER_OP2 = '1') then
58                 cu_next_state <= cu_load_op2;
59             elsif (CALCULATE = '1') then
60                 cu_next_state <= cu_run_calc0;
61             else
62                 cu_next_state <= cu_idle;
63             end if;
64         when cu_load_op1 =>
65             cu_next_state <= cu_idle;
66         when cu_load_op2 =>
67             cu_next_state <= cu_idle;
68         when cu_run_calc0 =>
69             cu_next_state <= cu_run_calc1;
70         when cu_run_calc1 =>
71             cu_next_state <= cu_run_calc2;
72         when cu_run_calc2 =>
73             cu_next_state <= cu_run_calc3;
74         when cu_run_calc3 =>
75             cu_next_state <= cu_finish;
76         when cu_finish =>
77             cu_next_state <= cu_finish;
78         when others =>
79             cu_next_state <= cu_idle;
80     end case;
```

```

81     end process;
82
83
84     CU_OUTPUT_DECODE: process (cu_cur_state)
85     begin
86         case(cu_cur_state) is
87             when cu_rst =>
88                 IN_SEL      <= "00";
89                 OP_CODE_BUS <= "00";
90                 RAM_ADDR_BUS <= "00";
91                 RAM_WR      <= '0';
92                 ACC_RST     <= '1';
93                 ACC_WR      <= '0';
94             when cu_idle =>
95                 IN_SEL      <= "00";
96                 OP_CODE_BUS <= "00";
97                 RAM_ADDR_BUS <= "00";
98                 RAM_WR      <= '0';
99                 ACC_RST     <= '0';
100                ACC_WR      <= '0';
101             when cu_load_op1 =>
102                 IN_SEL      <= "00";
103                 OP_CODE_BUS <= "00";
104                 RAM_ADDR_BUS <= "00";
105                 RAM_WR      <= '1';
106                 ACC_RST     <= '0';
107                 ACC_WR      <= '1';
108             when cu_load_op2 =>
109                 IN_SEL      <= "00";
110                 OP_CODE_BUS <= "00";
111                 RAM_ADDR_BUS <= "01";
112                 RAM_WR      <= '1';
113                 ACC_RST     <= '0';
114                 ACC_WR      <= '1';
115             when cu_run_calc0 =>
116                 IN_SEL      <= "01";
117                 OP_CODE_BUS <= "00";
118                 RAM_ADDR_BUS <= "01";
119                 RAM_WR      <= '0';
120                 ACC_RST     <= '0';
121                 ACC_WR      <= '1';
122             when cu_run_calc1 =>
123                 IN_SEL      <= "10";
124                 OP_CODE_BUS <= "10";
125                 RAM_ADDR_BUS <= "00";
126                 RAM_WR      <= '0';
127                 ACC_RST     <= '0';
128                 ACC_WR      <= '1';
129             when cu_run_calc2 =>
130                 IN_SEL      <= "01";
131                 OP_CODE_BUS <= "01";
132                 RAM_ADDR_BUS <= "00";
133                 RAM_WR      <= '0';
134                 ACC_RST     <= '0';
135                 ACC_WR      <= '1';
136             when cu_run_calc3 =>
137                 IN_SEL      <= "11";
138                 OP_CODE_BUS <= "11";
139                 RAM_ADDR_BUS <= "00";
140                 RAM_WR      <= '0';
141                 ACC_RST     <= '0';
142                 ACC_WR      <= '1';
143             when cu_finish =>
144                 IN_SEL      <= "00";
145                 OP_CODE_BUS <= "00";
146                 RAM_ADDR_BUS <= "00";
147                 RAM_WR      <= '0';
148                 ACC_RST     <= '0';
149                 ACC_WR      <= '0';
150             when others =>
151                 IN_SEL      <= "00";
152                 OP_CODE_BUS <= "00";
153                 RAM_ADDR_BUS <= "00";
154                 RAM_WR      <= '0';
155                 ACC_RST     <= '0';
156                 ACC_WR      <= '0';
157         end case;
158     end process;
159
160 end my_CU_arch;

```

Рис.4. Реалізація пристрою керування (CU) у файлі CU.vhd


## 5) Створив файл RAM.vhd.

```

1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3  use IEEE.STD_LOGIC_UNSIGNED.ALL;
4
5  entity my_RAM_intf is
6  port (
7      CLOCK          : in std_logic;
8      RAM_WR         : in std_logic;
9      RAM_ADDR_BUS    : in STD_LOGIC_VECTOR (1 downto 0);
10     RAM_DATA_IN_BUS  : in STD_LOGIC_VECTOR (7 downto 0);
11     RAM_DATA_OUT_BUS : out STD_LOGIC_VECTOR (7 downto 0)
12 );
13 end my_RAM_intf;
14
15 architecture my_RAM_arch of my_RAM_intf is
16
17     type ram_type is array (3 downto 0) of STD_LOGIC_VECTOR (7 downto 0);
18     signal RAM_UNIT : ram_type;
19
20 begin
21
22     RAM : process (CLOCK, RAM_ADDR_BUS, RAM_UNIT)
23     begin
24         if (rising_edge (CLOCK)) then
25             if (RAM_WR = '1') then
26                 RAM_UNIT (conv_integer (RAM_ADDR_BUS)) <= RAM_DATA_IN_BUS;
27             end if;
28         end if;
29         RAM_DATA_OUT_BUS <= RAM_UNIT (conv_integer (RAM_ADDR_BUS));
30     end process RAM;
31
32
33 end my_RAM_arch;
34

```

Рис.5. Реалізація пам'яті пристрою (RAM) у файлі RAM.vhd

 

Симуляція роботи RAM



5) Створив файл OUT\_PUT\_DECODER.vhd і реалізував в ньому блок індикації (7-SEG DECODER).

```

1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3  use IEEE.NUMERIC_STD.ALL;
4  use IEEE.STD_LOGIC_UNSIGNED.ALL;
5
6  entity OUT_PUT_DECODER_intf is
7  port(
8  CLOCK          : IN STD_LOGIC;
9  RESET          : IN STD_LOGIC;
10 ACC_DATA_OUT_BUS : IN std_logic_vector(7 downto 0);
11
12 COMM_ONES      : OUT STD_LOGIC;
13 COMM_DECS      : OUT STD_LOGIC;
14 COMM_HUNDREDS  : OUT STD_LOGIC;
15 SEG_A          : OUT STD_LOGIC;
16 SEG_B          : OUT STD_LOGIC;
17 SEG_C          : OUT STD_LOGIC;
18 SEG_D          : OUT STD_LOGIC;
19 SEG_E          : OUT STD_LOGIC;
20 SEG_F          : OUT STD_LOGIC;
21 SEG_G          : OUT STD_LOGIC;
22 DP             : OUT STD_LOGIC
23 );
24 end OUT_PUT_DECODER_intf;
25
26 architecture OUT_PUT_DECODER_arch of OUT_PUT_DECODER_intf is
27 signal ONES_BUS : STD_LOGIC_VECTOR(3 downto 0) := "0000";
28 signal DECS_BUS : STD_LOGIC_VECTOR(3 downto 0) := "0001";
29 signal HONDREDS_BUS : STD_LOGIC_VECTOR(3 downto 0) := "0000";
30
31 begin
32
33     BIN_TO_BCD : process (ACC_DATA_OUT_BUS)
34         variable hex_src : STD_LOGIC_VECTOR(7 downto 0) ;
35         variable bcd      : STD_LOGIC_VECTOR(11 downto 0) ;
36     begin
37         bcd      := (others => '0') ;
38         hex_src  := ACC_DATA_OUT_BUS;
39
40         for i in hex_src'range loop
41             if bcd(3 downto 0) > "0100" then
42                 bcd(3 downto 0) := bcd(3 downto 0) + "0011" ;
43             end if ;
44             if bcd(7 downto 4) > "0100" then
45                 bcd(7 downto 4) := bcd(7 downto 4) + "0011" ;
46             end if ;
47             if bcd(11 downto 8) > "0100" then
48                 bcd(11 downto 8) := bcd(11 downto 8) + "0011" ;
49             end if ;
50
51             bcd := bcd(10 downto 0) & hex_src(hex_src'left) ; -- shift bcd + 1
52             hex_src := hex_src(hex_src'left - 1 downto hex_src'right) & '0' ;
53         end loop ;
54
55         HONDREDS_BUS <= bcd (11 downto 8);
56         DECS_BUS    <= bcd (7 downto 4);
57         ONES_BUS    <= bcd (3 downto 0);
58
59     end process BIN_TO_BCD;
60
61     INDICATE : process (CLOCK)
62         type DIGIT_TYPE is (ONES, DECS, HUNDREDS);
63
64         variable CUR_DIGIT      : DIGIT_TYPE := ONES;
65         variable DIGIT_VAL      : STD_LOGIC_VECTOR(3 downto 0) := "0000";
66         variable DIGIT_CTRL     : STD_LOGIC_VECTOR(6 downto 0) := "0000000";
67         variable COMMONS_CTRL  : STD_LOGIC_VECTOR(2 downto 0) := "000";
68
69     begin
70         if (rising_edge(CLOCK)) then
71             if(RESET = '0') then
72                 case CUR_DIGIT is
73                     when ONES =>
74                         DIGIT_VAL := ONES_BUS;
75                         CUR_DIGIT := DECS;
76                         COMMONS_CTRL := "001";
77                     when DECS =>
78                         DIGIT_VAL := DECS_BUS;
79                         CUR_DIGIT := HUNDREDS;
80                         COMMONS_CTRL := "010";

```

```

81         when HUNDREDS =>
82             DIGIT_VAL := HONDREDS_BUS;
83             CUR_DIGIT := ONES;
84             COMMONS_CTRL := "100";
85         when others =>
86             DIGIT_VAL := ONES_BUS;
87             CUR_DIGIT := ONES;
88             COMMONS_CTRL := "000";
89     end case;
90
91     case DIGIT_VAL is
92         when "0000" => DIGIT_CTRL := "1111110";
93         when "0001" => DIGIT_CTRL := "0110000";
94         when "0010" => DIGIT_CTRL := "1101101";
95         when "0011" => DIGIT_CTRL := "1111001";
96         when "0100" => DIGIT_CTRL := "0110011";
97         when "0101" => DIGIT_CTRL := "1011011";
98         when "0110" => DIGIT_CTRL := "1011111";
99         when "0111" => DIGIT_CTRL := "1110000";
100        when "1000" => DIGIT_CTRL := "1111111";
101        when "1001" => DIGIT_CTRL := "1111011";
102        when others => DIGIT_CTRL := "0000000";
103    end case;
104    else
105        DIGIT_VAL := ONES_BUS;
106        CUR_DIGIT := ONES;
107        COMMONS_CTRL := "000";
108    end if;
109
110    COMM_ONES    <= COMMONS_CTRL(0);
111    COMM_DECS    <= COMMONS_CTRL(1);
112    COMM_HUNDREDS <= COMMONS_CTRL(2);
113
114    SEG_A <= DIGIT_CTRL(6);
115    SEG_B <= DIGIT_CTRL(5);
116    SEG_C <= DIGIT_CTRL(4);
117    SEG_D <= DIGIT_CTRL(3);
118    SEG_E <= DIGIT_CTRL(2);
119    SEG_F <= DIGIT_CTRL(1);
120    SEG_G <= DIGIT_CTRL(0);
121    DP    <= '0';
122
123    end if;
124    end process INDICATE;
125
126
127 end OUT_PUT_DECODER_arch;

```

Рис.6. Реалізація блоку індикації (7-SEG DECODER) в файлі  
OUT\_PUT\_DECODER.vhd

6) Згенерував символи для імплементованих компонентів і створив схему у файлі Top\_level.sch.

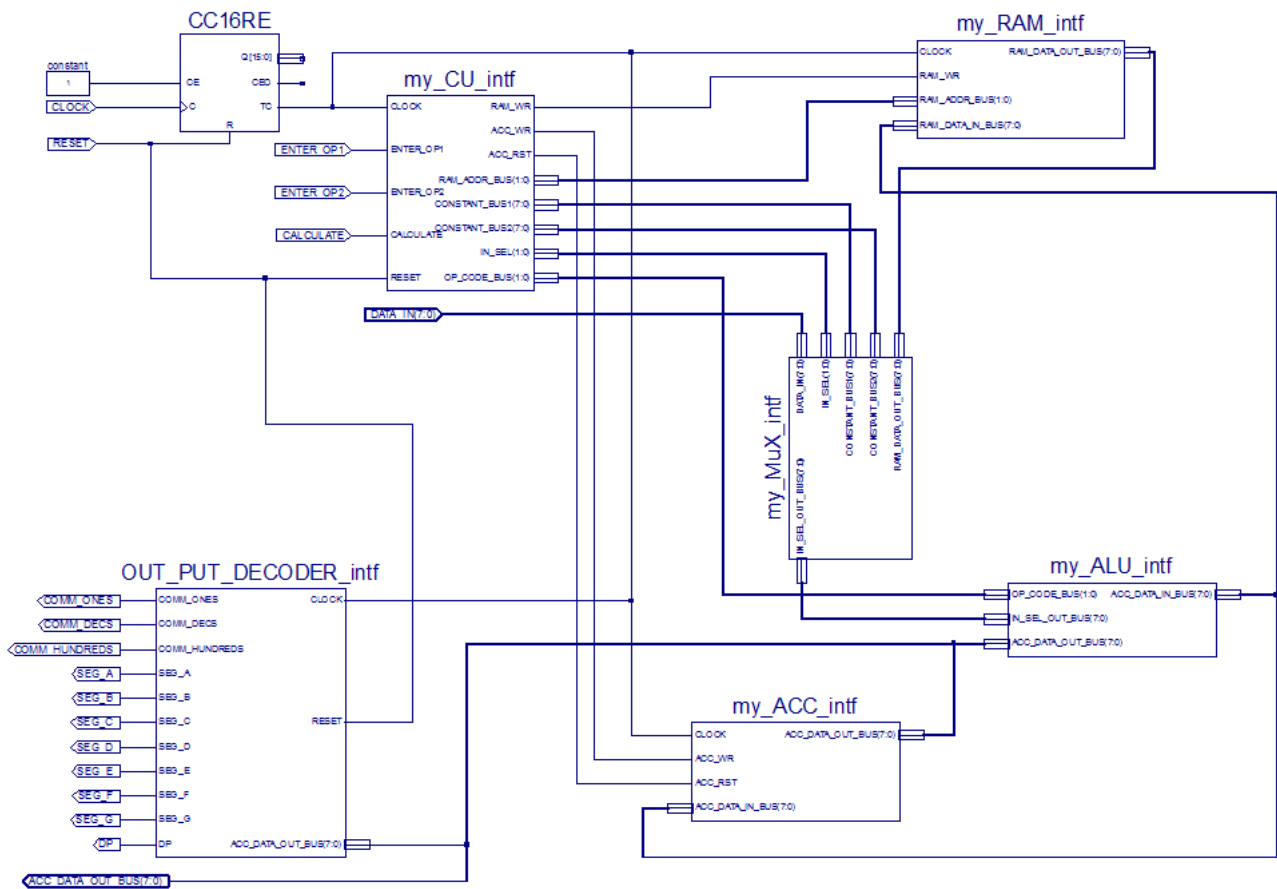


Рис.7. Схема з використанням імплементованих компонентів.

## 7) testbench.vhd.

```
1  LIBRARY ieee;
2  USE ieee.std_logic_1164.ALL;
3  USE ieee.numeric_std.ALL;
4  LIBRARY UNISIM;
5  USE UNISIM.vcomponents.ALL;
6  ENTITY TopLevel_TopLevel_sch_tb IS
7  END TopLevel_TopLevel_sch_tb;
8  ARCHITECTURE behavioral OF TopLevel_TopLevel_sch_tb IS
9
10     COMPONENT TopLevel
11     PORT( RESET : IN STD_LOGIC;
12           ACC_DATA_OUT_BUS : OUT STD_LOGIC_VECTOR (7 DOWNTO 0);
13           CLOCK : IN STD_LOGIC;
14           ENTER_OP1 : IN STD_LOGIC;
15           ENTER_OP2 : IN STD_LOGIC;
16           CALCULATE : IN STD_LOGIC;
17           DATA_IN : IN STD_LOGIC_VECTOR (7 DOWNTO 0);
18           COMM_ONES : OUT STD_LOGIC;
19           COMM_DECS : OUT STD_LOGIC;
20           COMM_HUNDREDS : OUT STD_LOGIC;
21           SEG_A : OUT STD_LOGIC;
22           SEG_B : OUT STD_LOGIC;
23           SEG_C : OUT STD_LOGIC;
24           SEG_D : OUT STD_LOGIC;
25           SEG_E : OUT STD_LOGIC;
26           SEG_F : OUT STD_LOGIC;
27           SEG_G : OUT STD_LOGIC;
28           DP : OUT STD_LOGIC);
29     END COMPONENT;
30
31
32     SIGNAL op1 : STD_LOGIC_VECTOR(7 DOWNTO 0);
33     SIGNAL op2 : STD_LOGIC_VECTOR(7 DOWNTO 0);
34     SIGNAL RESET : STD_LOGIC;
35     SIGNAL CLOCK : STD_LOGIC;
36     SIGNAL ENTER_OP1 : STD_LOGIC;
37     SIGNAL ENTER_OP2 : STD_LOGIC;
38     SIGNAL CALCULATE : STD_LOGIC;
39     SIGNAL DATA_IN : STD_LOGIC_VECTOR (7 DOWNTO 0);
40     SIGNAL COMM_ONES : STD_LOGIC;
41     SIGNAL COMM_DECS : STD_LOGIC;
42     SIGNAL COMM_HUNDREDS : STD_LOGIC;
43     SIGNAL SEG_A : STD_LOGIC;
44     SIGNAL SEG_B : STD_LOGIC;
45     SIGNAL SEG_C : STD_LOGIC;
46     SIGNAL SEG_D : STD_LOGIC;
47     SIGNAL SEG_E : STD_LOGIC;
48     SIGNAL SEG_F : STD_LOGIC;
49     SIGNAL SEG_G : STD_LOGIC;
50     SIGNAL DP : STD_LOGIC;
51     SIGNAL ACC_DATA_OUT_BUS : STD_LOGIC_VECTOR (7 DOWNTO 0);
52
53
54     constant CLK_period: time := 1 us;
55     constant TC_period: time := 65536 us;
56
57
58 BEGIN
59
60     UUT: TopLevel PORT MAP(
61         RESET => RESET,
62         ACC_DATA_OUT_BUS => ACC_DATA_OUT_BUS,
63         CLOCK => CLOCK,
64         ENTER_OP1 => ENTER_OP1,
65         ENTER_OP2 => ENTER_OP2,
66         CALCULATE => CALCULATE,
67         DATA_IN => DATA_IN,
68         COMM_ONES => COMM_ONES,
69         COMM_DECS => COMM_DECS,
70         COMM_HUNDREDS => COMM_HUNDREDS,
71         SEG_A => SEG_A,
72         SEG_B => SEG_B,
73         SEG_C => SEG_C,
74         SEG_D => SEG_D,
75         SEG_E => SEG_E,
76         SEG_F => SEG_F,
77         SEG_G => SEG_G,
78         DP => DP
79     );
80
```

```
81 CLK_process : process
82   begin
83     CLOCK <= '1';
84     wait for CLK_period/2;
85     CLOCK <= '0';
86     wait for CLK_period/2;
87   end process CLK_process;
88
89   stim_proc: process
90   begin
91     RESET <= '1';
92     ENTER_OP1 <= '0';
93     ENTER_OP2 <= '0';
94     CALCULATE <= '0';
95     DATA_IN  <=(others => '0');
96
97     wait for 2*CLK_period;
98     RESET <='0';
99
100    wait for 4*TC_period;
101    ENTER_OP1 <='1';
102    DATA_IN  <= op1;
103
104    wait for 2*TC_period;
105    ENTER_OP1 <='0';
106
107    wait for 4*TC_period;
108    ENTER_OP2 <='1';
109    DATA_IN  <= op2;
110
111    wait for 2*TC_period;
112    ENTER_OP2 <='0';
113    wait for 4*TC_period;
114
115    CALCULATE <= '1';
116    wait for 8*TC_period;
117    wait;
118  end process stim_proc; --1.835 s
119
120 END;
```

---

## 8) Constraints

```

1  |*****
2  |#
3  |# UCF for ElbertV2 Development Board
4  |*****
5  |CONFIG VCCAUX = "3.3" ;
6  |
7  |# Clock 12 MHz
8  |NET "CLOCK"          LOC = P129 | IOSTANDARD = LVCMOS33 | PERIOD = 12MHz;
9  |
10 |*****
11 |# Seven Segment Display
12 |*****
13 |NET "SEG_A"          LOC = P117 | IOSTANDARD = LVCMOS33 | SLEW = SLOW | DRIVE = 12;
14 |NET "SEG_B"          LOC = P116 | IOSTANDARD = LVCMOS33 | SLEW = SLOW | DRIVE = 12;
15 |NET "SEG_C"          LOC = P115 | IOSTANDARD = LVCMOS33 | SLEW = SLOW | DRIVE = 12;
16 |NET "SEG_D"          LOC = P113 | IOSTANDARD = LVCMOS33 | SLEW = SLOW | DRIVE = 12;
17 |NET "SEG_E"          LOC = P112 | IOSTANDARD = LVCMOS33 | SLEW = SLOW | DRIVE = 12;
18 |NET "SEG_F"          LOC = P111 | IOSTANDARD = LVCMOS33 | SLEW = SLOW | DRIVE = 12;
19 |NET "SEG_G"          LOC = P110 | IOSTANDARD = LVCMOS33 | SLEW = SLOW | DRIVE = 12;
20 |NET "DP"             LOC = P114 | IOSTANDARD = LVCMOS33 | SLEW = SLOW | DRIVE = 12;
21 |
22 |NET "COMM_HUNDREDS"   LOC = P124 | IOSTANDARD = LVCMOS33 | SLEW = SLOW | DRIVE = 12;
23 |NET "COMM_DECS"      LOC = P121 | IOSTANDARD = LVCMOS33 | SLEW = SLOW | DRIVE = 12;
24 |NET "COMM_ONES"      LOC = P120 | IOSTANDARD = LVCMOS33 | SLEW = SLOW | DRIVE = 12;
25 |*****
26 |# DP Switches
27 |*****
28 |
29 |NET "DATA_IN(0)"      LOC = P70 | PULLUP | IOSTANDARD = LVCMOS33 | SLEW = SLOW | DRIVE = 12;
30 |NET "DATA_IN(1)"      LOC = P69 | PULLUP | IOSTANDARD = LVCMOS33 | SLEW = SLOW | DRIVE = 12;
31 |NET "DATA_IN(2)"      LOC = P68 | PULLUP | IOSTANDARD = LVCMOS33 | SLEW = SLOW | DRIVE = 12;
32 |NET "DATA_IN(3)"      LOC = P64 | PULLUP | IOSTANDARD = LVCMOS33 | SLEW = SLOW | DRIVE = 12;
33 |NET "DATA_IN(4)"      LOC = P63 | PULLUP | IOSTANDARD = LVCMOS33 | SLEW = SLOW | DRIVE = 12;
34 |NET "DATA_IN(5)"      LOC = P60 | PULLUP | IOSTANDARD = LVCMOS33 | SLEW = SLOW | DRIVE = 12;
35 |NET "DATA_IN(6)"      LOC = P59 | PULLUP | IOSTANDARD = LVCMOS33 | SLEW = SLOW | DRIVE = 12;
36 |NET "DATA_IN(7)"      LOC = P58 | PULLUP | IOSTANDARD = LVCMOS33 | SLEW = SLOW | DRIVE = 12;
37 |
38 |*****
39 |# Switches
40 |*****
41 |
42 |NET "ENTER_OP1"       LOC = P80 | PULLUP | IOSTANDARD = LVCMOS33 | SLEW = SLOW | DRIVE = 12;
43 |NET "ENTER_OP2"       LOC = P79 | PULLUP | IOSTANDARD = LVCMOS33 | SLEW = SLOW | DRIVE = 12;
44 |NET "CALCULATE"        LOC = P78 | PULLUP | IOSTANDARD = LVCMOS33 | SLEW = SLOW | DRIVE = 12;
45 |NET "RESET"           LOC = P75 | PULLUP | IOSTANDARD = LVCMOS33 | SLEW = SLOW | DRIVE = 12;
46 |

```


 


Рис.8. Часова діаграма згідно методичних вказівок.

 

### Перевірка:

$((OP2 - 4) + OP1) \text{ or } 2$

$OP1 \Rightarrow 0000\ 1101$

$OP2 \Rightarrow 0001\ 0100$

$((0001\ 0100 - 0000\ 0100) + 0000\ 1101) \text{ or } 0000\ 0010$

$0001\ 0100 - 0000\ 0100 = 0001\ 0000$

$0001\ 0000 + 0000\ 1101 = 0001\ 1101$

$0001\ 1101 \text{ or }$

$0000\ 0010 = 0001\ 1111$

### Висновок:

На цій лабораторній роботі реалізував цифровий автомат для обчислення значення виразу та симулював його роботу.